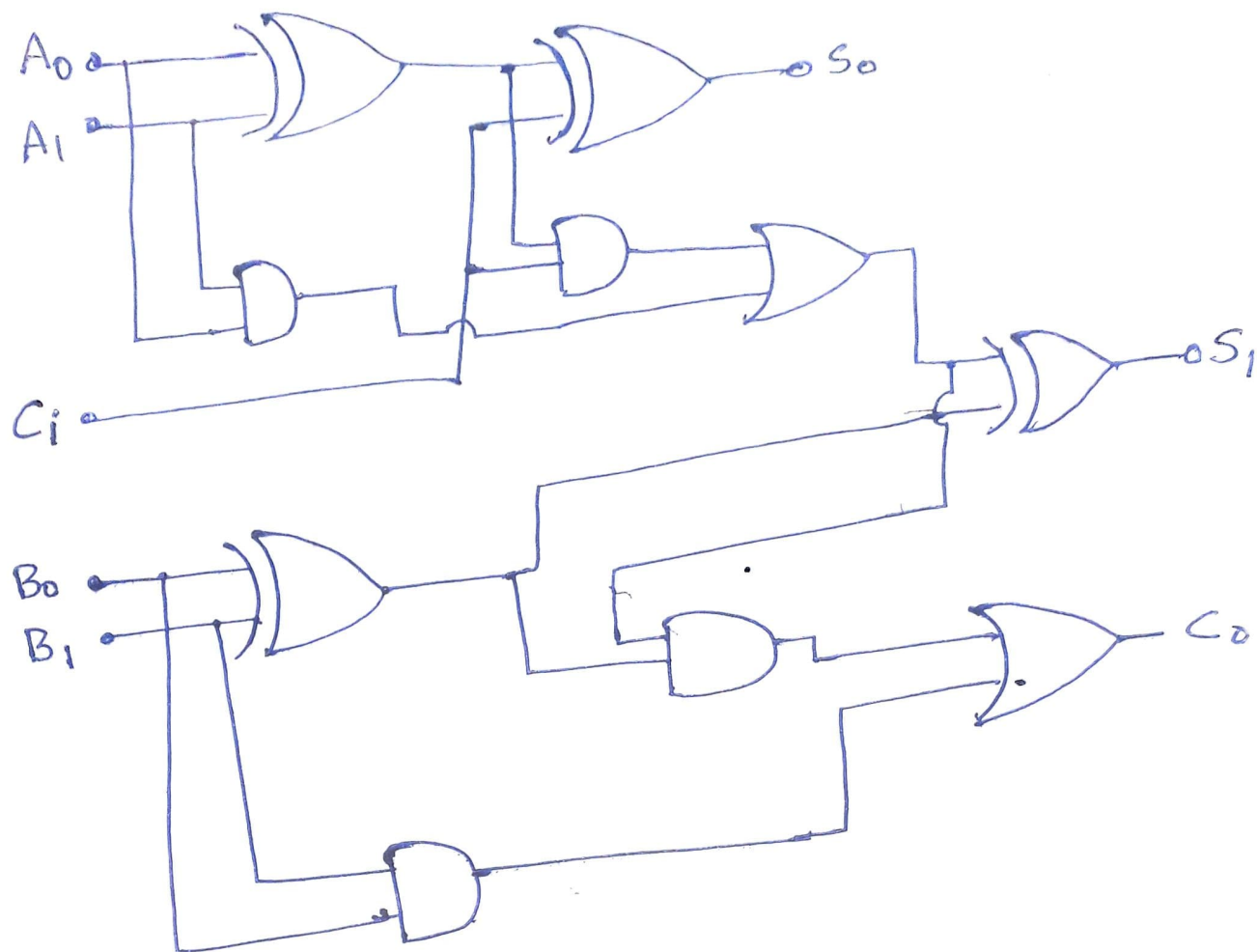


② 2-bit full adder.



~~also~~ Boolean Equations

①

$$S_0 = A_0 \oplus A_1 \oplus C_i$$


$$S_1 = B_0 \oplus B_1 \oplus [A_0 A_1 + C_i [A_0 \oplus A_1]]$$

$$C_0 = B_0 B_1 + [A_0 A_1 + C_i [A_0 \oplus A_1]] [B_0 \oplus B_1]$$

Explanation

A is anded with not(B) and C is anded with not(D) product the terms are "Ored" together is the only possible solution.

correct PLA fuse pattern

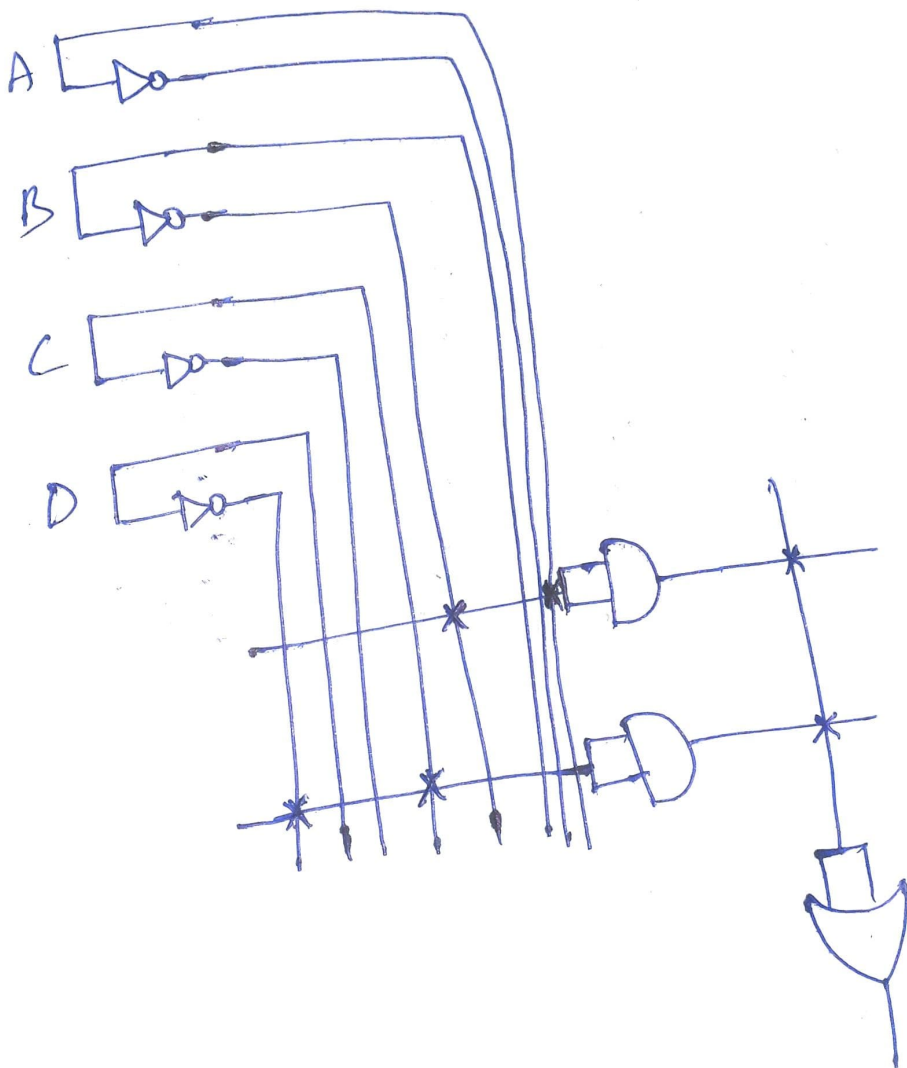

$$F = (A + B) * (C + D)$$

$$F = AB' + CD'$$

Addr		RAM contents		Output data
A	B	C	D	addr F
0	0	0	0	0
0	0	0	1	0
0	0	1	0	1
0	0	1	1	0
0	1	0	0	0
0	1	0	1	0
0	1	1	0	1
0	1	1	1	0
1	0	0	0	1
1	0	0	1	1
1	0	1	0	1
1	0	1	1	1
1	1	0	0	0
1	1	0	1	0
1	1	1	0	1
1	1	1	1	0